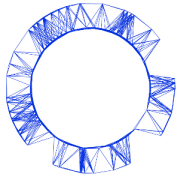


Experiment



IPhO 2018
Lisbon, Portugal

A1-1

English (Official)

Write down the numbers 0 to 9 in the following table:

0	1	2	3	4	5	6	7	8	9


Part A: Circuit Dimensioning (2.5 points)

A.1 (0.2 pt)

$V_{\text{out}} =$

A.2 (0.5 pt)

#	R_{T1}	R_{T2}	R_{T3}
\overline{R}			
σ_R			

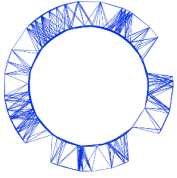

A.3 (0.3 pt)

Demonstration:

A.4 (0.4 pt)

$$R_{\square} = \quad \pm$$

$$\rho_{\text{Carbon film}} = \quad \pm$$

A.5 (0.5 pt)


Demonstration:

Measured values:

$$R_1 =$$

$$R_2 =$$

$$\kappa =$$

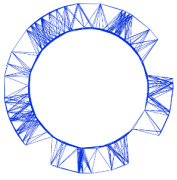


A.6 (0.3 pt)

R_1 Points	R_x	R_y	R_2 Points	R_x	R_y
Z			Z		
A			H		
B			I		
C			J		
D			K		
E			L		
F			M		
G			N		
V			W		

A.7 (0.3 pt)

Points	V_{out}	Points	V_{out}
A		H	
B		I	
C		J	
D		K	
E		L	
F		M	
G		N	
V		W	

Experiment

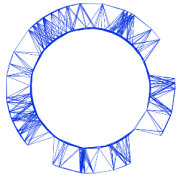

IPhO 2018
Lisbon, Portugal

A1-4

English (Official)

Part B: Characteristic Curves of the JFET transistor (4.5 points)

B.1 (0.2 pt)

$I_{DS} =$


B.2 (0.8 pt)

I_{DS} current values:


Gate/Drain	Z	H	I	J	K	L	M	N	W
Z									
A									
B									
C									
D									
E									
F									
G									
V									


B.3 (0.2 pt)

$f =$

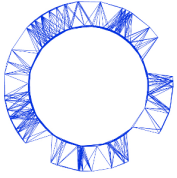

B.5 (0.5 pt)
Output curves:

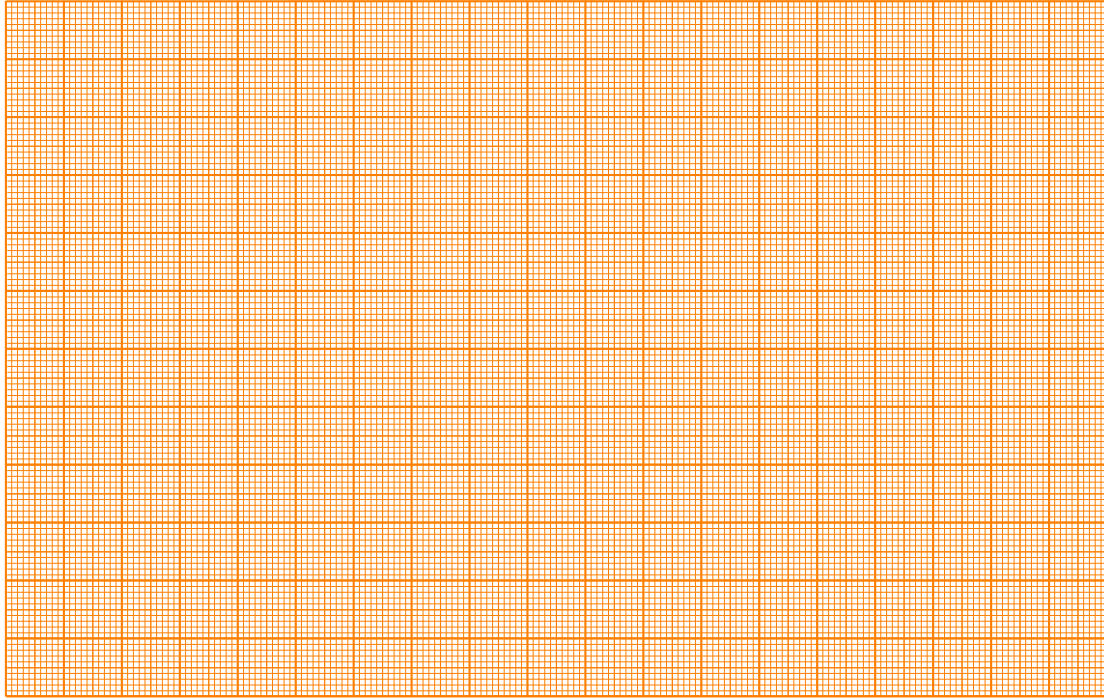


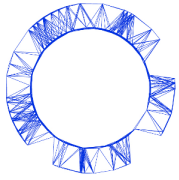


B.6 (0.5 pt)

V_{GS}	R_{DS}


Graph: $R_{DS}(V_{GS})$

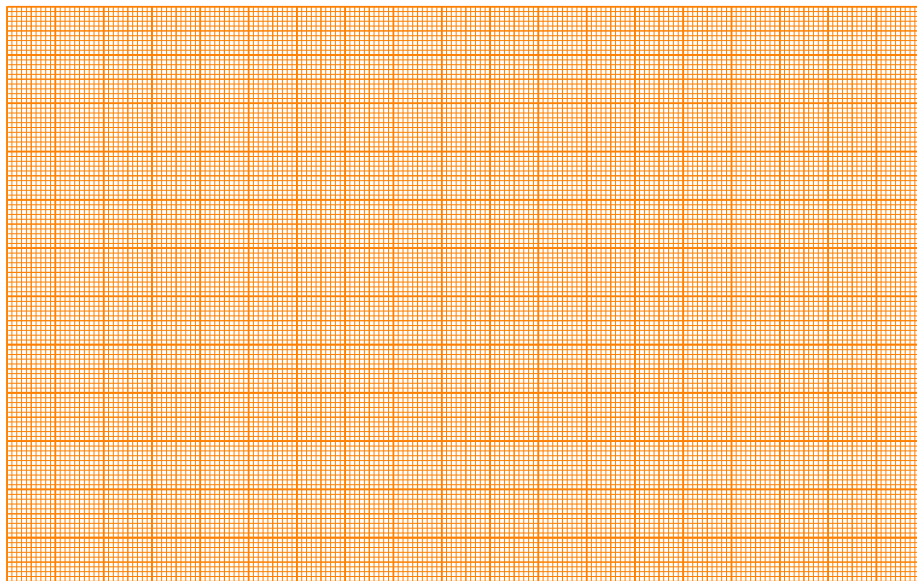

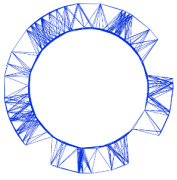

B.7 (0.3 pt)

Transfer curve:

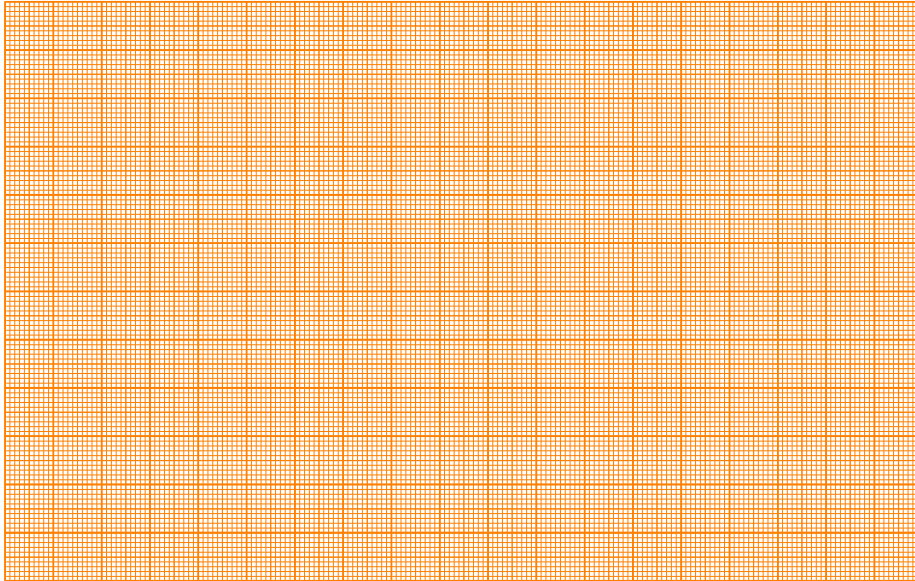

B.8 (0.4 pt)


$I_{DSS} =$

$V_P =$

B.9 (0.4 pt)


Measured transconductance: $g =$

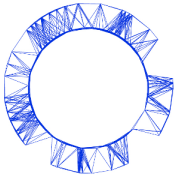Calculated transconductance from JFET model: $g =$




C.2 (1.2 pt)


Graph: $I_{DS}(t)$

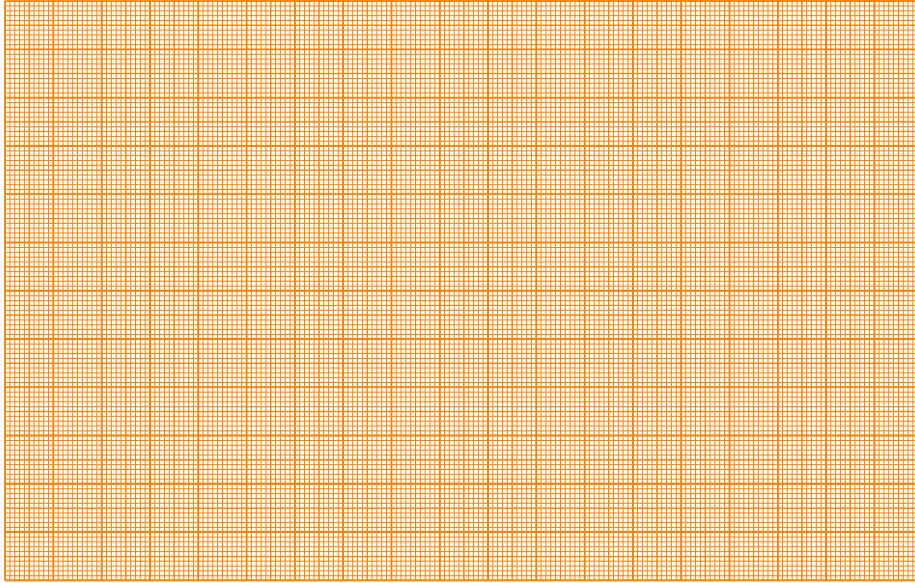

Auxiliary graph to determine τ_1 :

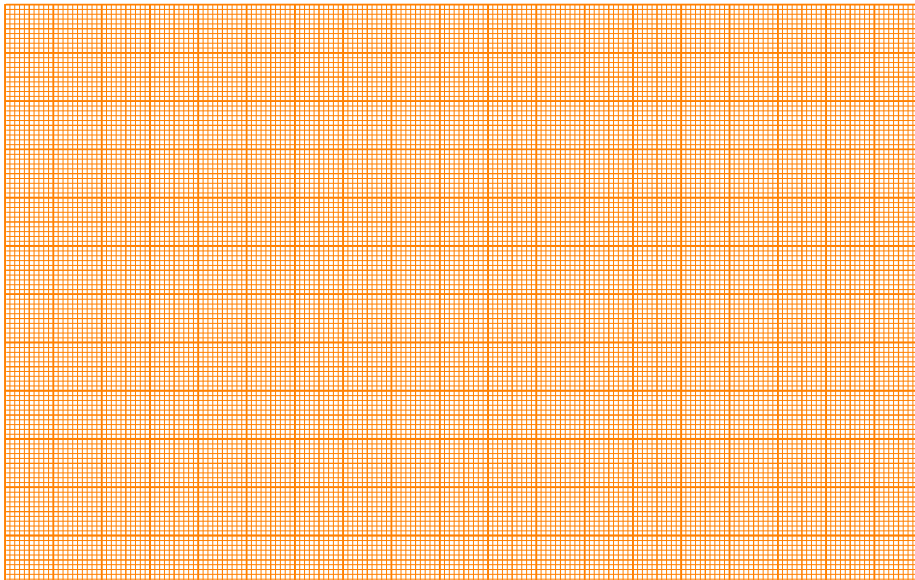

$\tau_1 =$

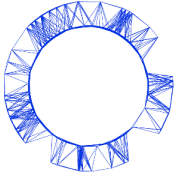

D.2 (0.5 pt)
Graph: $V_{\text{out}}(V_{\text{in}})$

