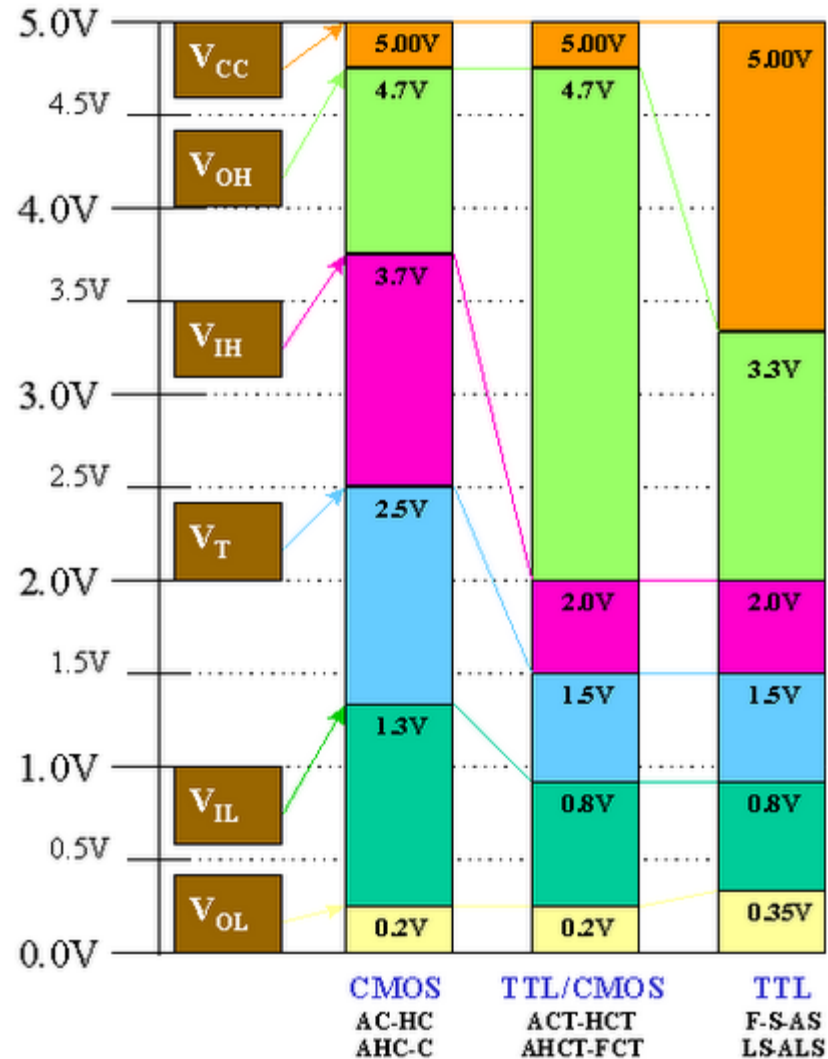



Logic Families Comparison

Family	Propagation delay (ns)	Power per gate @1 MHz (mW)	Typical supply voltage V	Notes
CMOS AC/ACT	3	0.5	3.3 or 5 (2-6 or 4.5 to 5.5)	ACT has TTL Compatible level
CMOS HC/HCT	9	0.5	5 (2-6)	HCT has TTL compatible levels
MOS 4000B/74C	30	1.2	10V (3-18)	
TTL	10	10	5 (4.75-5.25)	
TTL L	33	1	..	
TTL H	6	22	..	
TTL S	3	19	..	
TTL LS	10	2	..	
TTL ALS	4	1.3	..	
TTL F	3.5	5.4	..	
TTL AS	2	8	..	
ECL 100K	.75	40	-5.2(-4.9 - -5.5)	

Logic Families Voltage Levels



Input Output Standards

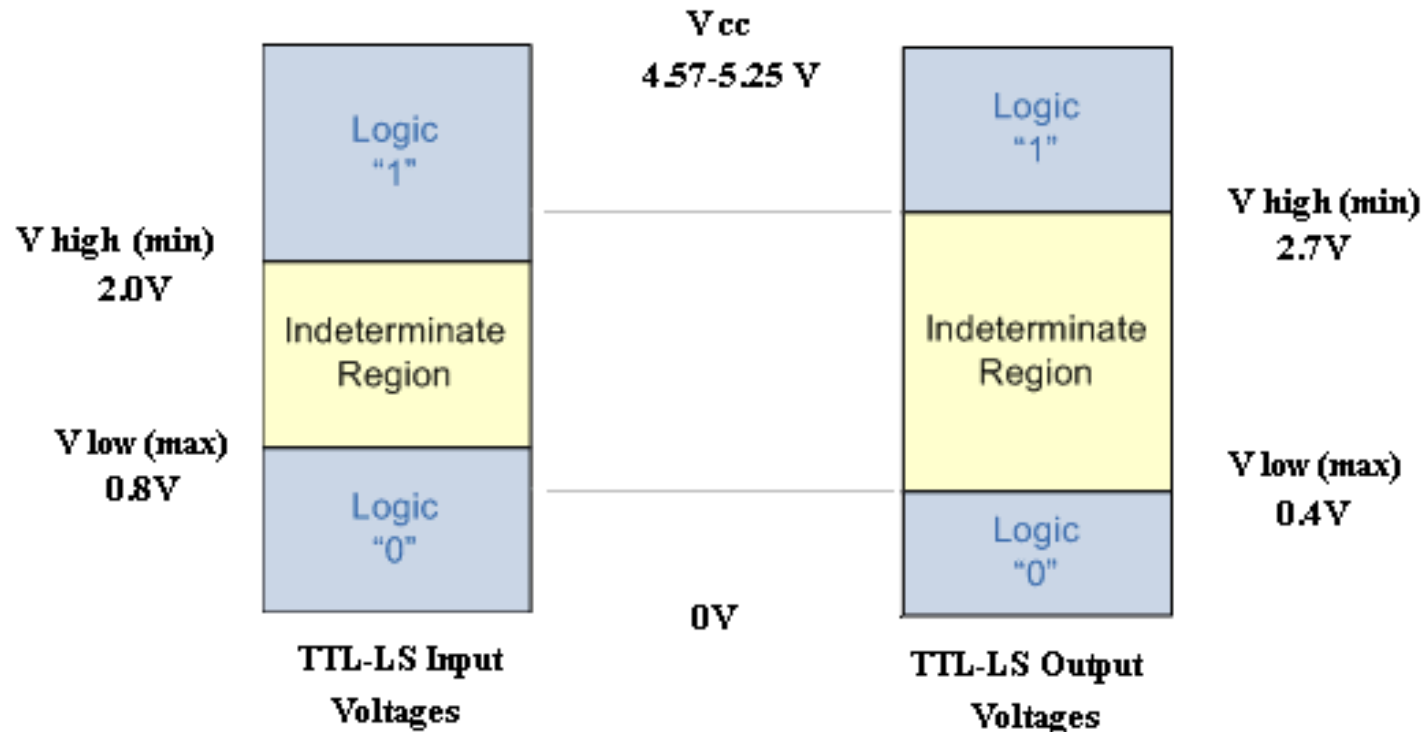

Logic Circuits Interfacing


Many applications require mixing logic families:

Different voltage levels

→ Level shifting circuits

→ Current driving


ECL to TTL

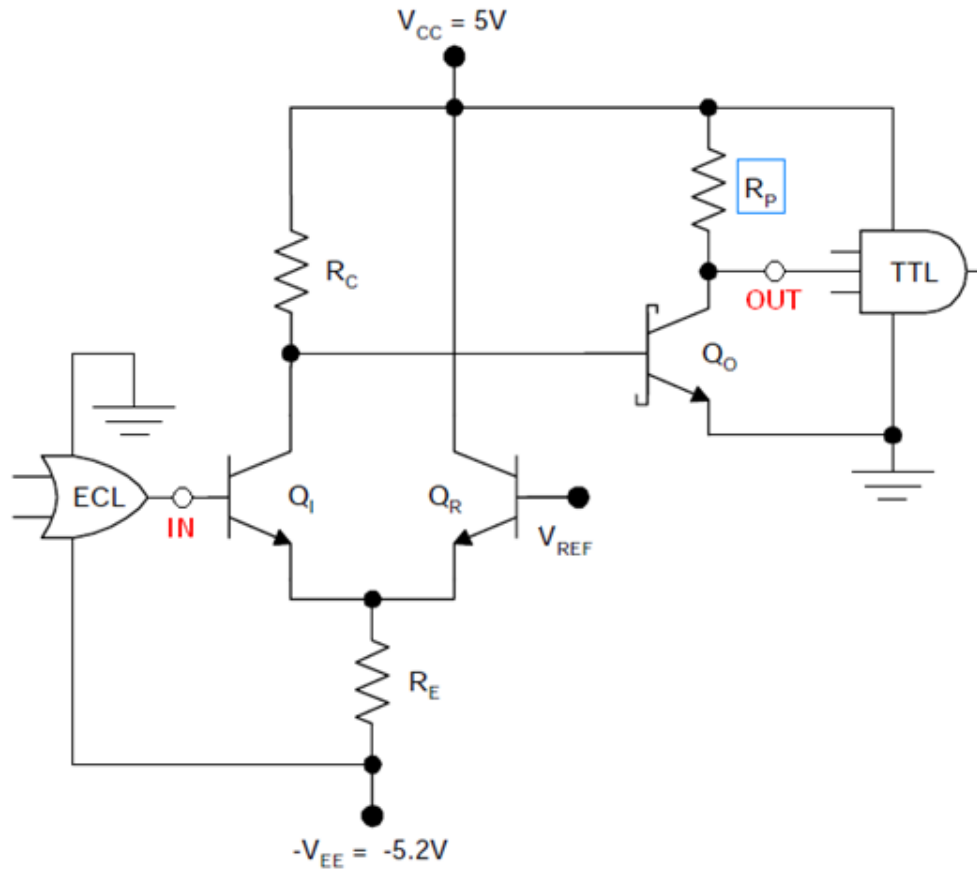

$V_{IN} = V_{OL}(\text{ECL}) \rightarrow Q_1 \text{ off} \rightarrow Q_0 \text{ on hard} \rightarrow \text{OUT} = V_{CE} = V_{OL}(\text{TTL})$

$V_{IN} = V_{OH}(\text{ECL}) \rightarrow Q_1 \text{ on} \rightarrow Q_0 \text{ off} \rightarrow \text{OUT} = V_{DD} = V_{OH}(\text{TTL})$


TTL to ECL

 

$$V_{IN} = V_{OL}(\text{TTL}) \rightarrow V_{BQI} < V_{REF} \rightarrow Q_1 \text{ off, } Q_R \text{ on} \rightarrow V_{OL}(\text{ECL})$$

$$V_{IN} = V_{OH}(\text{TTL}) \rightarrow Q_1 \text{ on, } Q_R \text{ off} \rightarrow V_{OH}(\text{ECL})$$

TTL to CMOS

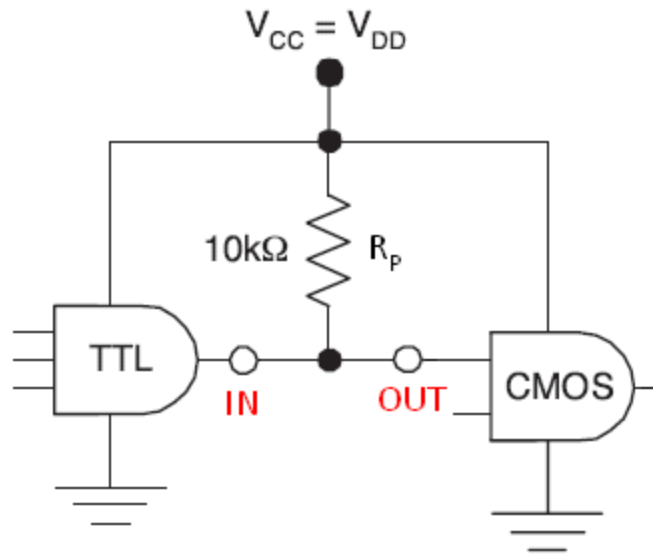


Simple because voltage levels are almost the same.

Pull-up resistor R_p forces OUT to V_{DD} .

Note: $V_{OH}(\text{TTL}) < V_{DD} - V_T(\text{CMOS})$

CMOS to TTL

 

(!)

Thank You
&
Best Wishes

Omar Alasali